

Digital Logic

CMSC 313

Raphael Elspas

Binary Logic definitions

- Binary variables take on one of two values.
- Logical operators operate on binary values and binary variables.
- Basic logical operators are the logic functions AND, OR and NOT.
- Logic gates implement logic functions.
- Boolean Algebra: a useful mathematical system for specifying and transforming logic functions.
- We study Boolean algebra as foundation for designing and analyzing digital systems!

Binary Variables

- **Just like a regular variable, except takes only two values**
- **Recall that the two binary values have different names:**
 - **True/False**
 - **On/Off**
 - **Yes/No**
 - **1/0**
- **We use 1 and 0 to denote the two values.**

Boolean Operators

- **AND**

- denoted by a dot (\cdot) or two variables immediately next to each other.
- $Y=A\cdot B$ is read “Y is equal to A AND B.”

- **OR**

- denoted by a plus (+).
- $z = x + y$ is read “z is equal to x OR y.”

- **NOT**

- denoted by an overbar ($\bar{\quad}$), a single quote mark (') after, or (\sim) before the variable.
- $X = \bar{A}$ is read “X is equal to NOT A.”

- **XOR**

- Denoted by a plus with a circle (\oplus)

Truth Tables

AND

X	Y	$X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

OR

X	Y	$X + Y$
0	0	0
0	1	1
1	0	1
1	1	1

NOT

X	\bar{X}
0	1
1	0

NAND

X	Y	$\overline{X \cdot Y}$
0	0	1
0	1	1
1	0	1
1	1	0

NOR


X	Y	$\overline{X + Y}$
0	0	1
0	1	0
1	0	0
1	1	0

XOR

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0


Gate Symbols

- Logic gates have special symbols:

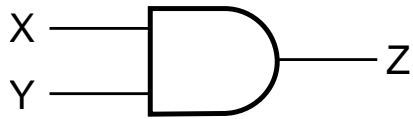


AND gate

$$XY = Z$$

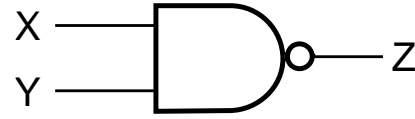


NAND gate

$$\overline{XY} = Z$$

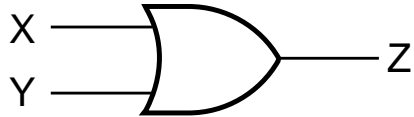


OR gate

$$X + Y = Z$$

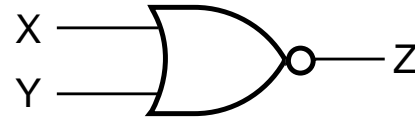


NOR gate

$$\overline{X + Y} = Z$$

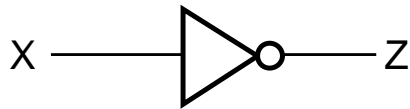

NOT gate or
inverter

$$\bar{X} = Z$$

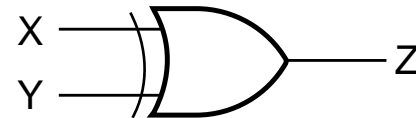


XOR gate

$$X \oplus Y = Z$$

Representation

- Boolean equations, truth tables and logic diagrams describe the same function!
- Truth tables are unique; expressions and logic diagrams are not. This gives flexibility in implementing functions.

x	y	z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

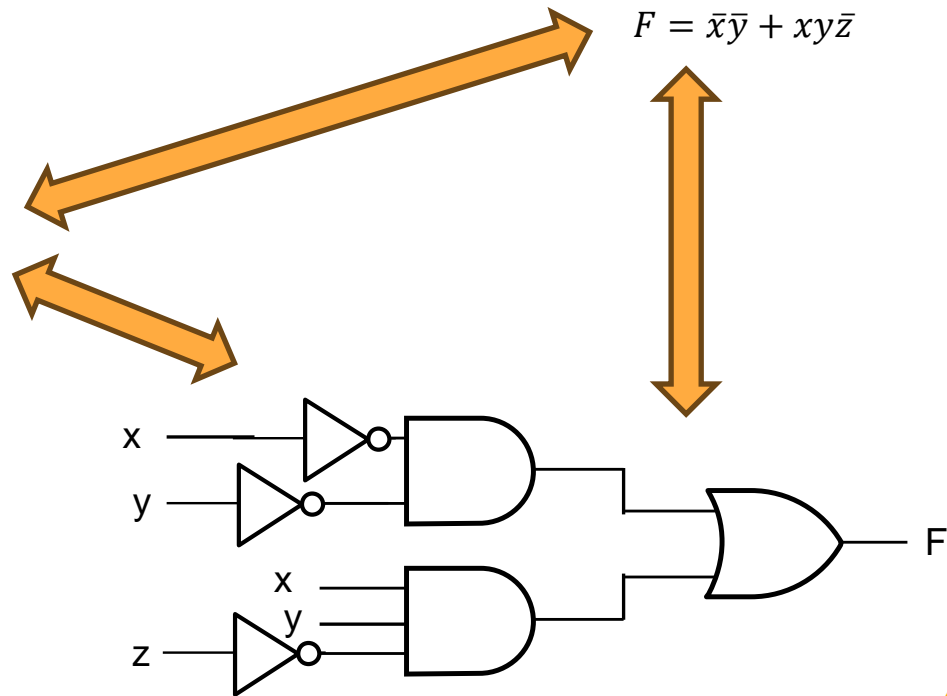

Order of Operations

- Order:
 1. Parentheses
 2. NOT
 3. AND
 4. OR
- Consequence: Parentheses appear around OR expressions
- Example: $F = A(B + C)(C + \bar{D})$
 1. \bar{D} : not
 2. $B + C$, $C + \bar{D}$: parenthesis
 3. $A(B + C)(C + \bar{D})$: and

Boolean Function Evaluation

$$F1 = xy\bar{z}$$

$$F2 = x + \bar{y}z$$


$$F3 = \bar{x}\bar{y}\bar{z} + \bar{x}yz + x\bar{y}$$

$$F4 = x\bar{y} + \bar{x}z$$


x	y	z	F1	F2	F3	F4
0	0	0	0	0	1	0
0	0	1	0	1	0	1
0	1	0	0	0	0	0
0	1	1	0	0	1	1
1	0	0	0	1	1	1
1	0	1	0	1	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	0

Logic Circuit Examples

- Example 1: Draw the circuit $XY+Z = F$

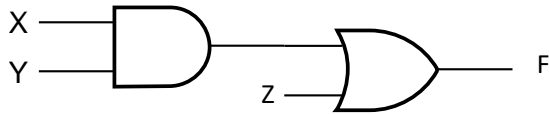


- Example 2: Find the Boolean expression

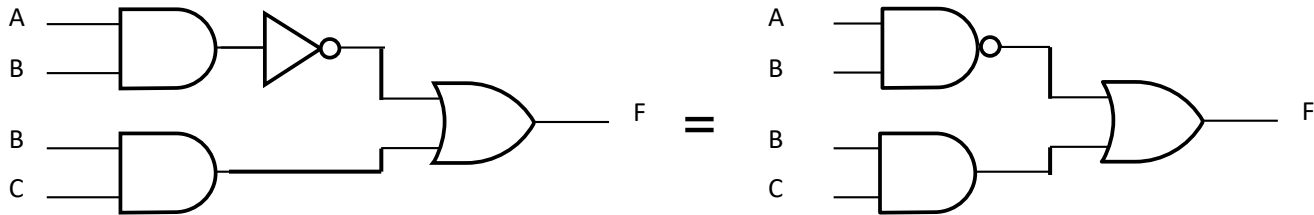

$$\overline{AB} + BC = F$$

Meme

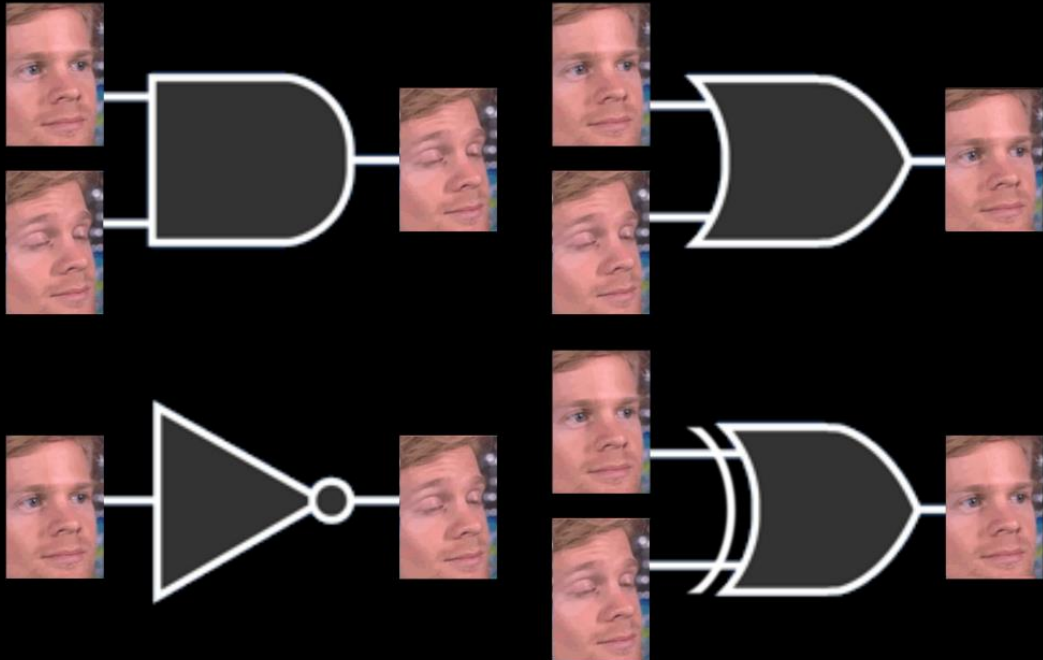The first logic gates must have been like:




Boolean Algebra Identities

1.	$X + 0 = X$	2.	$X \cdot 1 = X$	Identity
3.	$X + 1 = 1$	4.	$X \cdot 0 = 0$	Null Element
5.	$X + X = X$	6.	$X \cdot X = X$	Idempotence
7.	$X + \overline{X} = 1$	8.	$X \cdot \overline{X} = 0$	Complement
9.	$\overline{\overline{X}} = X$			Involution
<hr/>				
10.	$X + Y = Y + X$	11.	$XY = YX$	Commutative
12.	$(X + Y) + Z = X + (Y + Z)$	13.	$(XY)Z = X(YZ)$	Associative
14.	$X(Y + Z) = XY + XZ$	15.	$X + YZ = (X + Y)(X + Z)$	Distributive
16.	$\overline{X + Y} = \overline{X} \cdot \overline{Y}$	17.	$\overline{X \cdot Y} = \overline{X} + \overline{Y}$	DeMorgan's

Note: These are grouped as duals. The **dual** of an algebraic expression is obtained by interchanging + and \cdot and interchanging 0's and 1's.

Moar memes

Some guy named
William

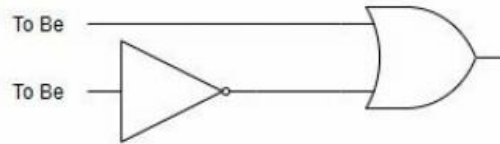

Me, an intellectual who
understands Boolean
algebra

1

$X + \sim X = 1$
Complement

How inefficient of him

Example 1: Boolean Algebraic Proof

- $A + A \cdot B = A$ (Absorption Theorem)

Proof Steps

$$\begin{aligned} & A + A \cdot B \\ = & A \cdot 1 + A \cdot B \\ = & A \cdot (1 + B) \\ = & A \cdot 1 \\ = & A \end{aligned}$$

Justification (identity or theorem)

$$\begin{aligned} X &= X \cdot 1 \quad (\text{Identity}) \\ X \cdot Y + X \cdot Z &= X \cdot (Y + Z) \quad (\text{Distributive Law}) \\ 1 + X &= 1 \quad (\text{Null element}) \\ X \cdot 1 &= X \quad (\text{Identity}) \end{aligned}$$

Example 2: Boolean Algebraic Proofs

- $AB + \bar{A}C + BC = AB + \bar{A}C$ (Consensus Theorem)


Proof Steps

Justification (identity or theorem)


$AB + \bar{A}C + BC$	
$= AB + \bar{A}C + 1 \cdot BC$	(identity)
$= AB + \bar{A}C + (A + \bar{A}) \cdot BC$	(complement)
$= AB + \bar{A}C + ABC + \bar{A}BC$	(Distributive Law)
$= AB + ABC + \bar{A}C + \bar{A}BC$	(Commutative Law)
$= AB \cdot 1 + ABC + \bar{A}C \cdot 1 + \bar{A}C \cdot B$	(identity, Commutative Law)
$= AB(1 + C) + \bar{A}C(1 + B)$	(Distributive Law)
$= AB \cdot 1 + \bar{A}C \cdot 1 = AB + \bar{A}C$	(identity)

DeMorgan's Law
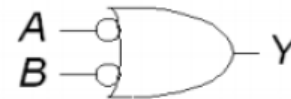
$$\overline{A \cdot B} = \bar{A} + \bar{B}$$


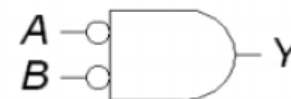
$$\overline{A + B} = \bar{A} \cdot \bar{B}$$



Proof of DeMorgan's Laws (part 1)

- Show the truth table of left and right side match

$$\overline{x + y} = \bar{x} \cdot \bar{y}$$

x	y	x + y	$\overline{x + y}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

x	y	\bar{x}	\bar{y}	$\bar{x} \cdot \bar{y}$
0	0	1	1	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	0

Proof of DeMorgan's Laws (part 2)

- Show the truth table of left and right side match

$$\overline{x \cdot y} = \bar{x} + \bar{y}$$

x	y	xy	\overline{xy}
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

x	y	\bar{x}	\bar{y}	$\bar{x} + \bar{y}$
0	0	1	1	1
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0

Useful Theorems

- **Minimization**

- $XY + \bar{X}Y = Y$
- $(X + Y)(\bar{X} + Y) = Y$

- **Absorption**

- $X + XY = X$
- $X(X + Y) = X$

- **Simplification**

- $X + \bar{X}Y = X + Y$
- $X(\bar{X} + Y) = XY$

- **Consensus**

- $AB + \bar{A}C + BC = AB + \bar{A}C$
- $(A + B)(\bar{A} + C)(B + C) = (A + B)(\bar{A} + C)$

Variables and Literals

- $F = xy + x\bar{y}z$
- There are **3 variables**: x, y, z
- There are **5 literals**: x, y, x, \bar{y}, z
 - Includes complements and duplicates

Expression Simplification

- Simplify to contain the smallest number of literals.

Example: $AB + \bar{A}CD + \bar{A}BD + \bar{A}\bar{C}\bar{D} + ABCD$

$$= AB + ABCD + \bar{A}CD + \bar{A}\bar{C}\bar{D} + \bar{A}BD$$

$$= AB(1 + CD) + \bar{A}C(D + \bar{D}) + \bar{A}BD \text{ (distributive)}$$

$$= AB + \bar{A}C(D + \bar{D}) + \bar{A}BD \text{ (Null Element)}$$

$$= AB + \bar{A}C + \bar{A}BD \text{ (Complement)}$$

$$= B(A + \bar{A}D) + \bar{A}C \text{ (distributive, commutative)}$$

$$= B(A + D) + \bar{A}C \text{ (Simplification Theorem)}$$

Complementing Functions

- Sometime useful for a circuit to use more AND then OR gates or vice versa
- Use DeMorgan's
- Example: Complement $F = \bar{x} y z + x \bar{y} \bar{z}$


$$\begin{aligned}\bar{F} &= \overline{\bar{x} y z + x \bar{y} \bar{z}} \\ &= (\overline{\bar{x} y z}) (\overline{x \bar{y} \bar{z}}) \\ &= (x + \bar{y} + z) (\bar{y} + y + \bar{z})\end{aligned}$$

Complementing Circuits

- Bubble Pushing


Steps:

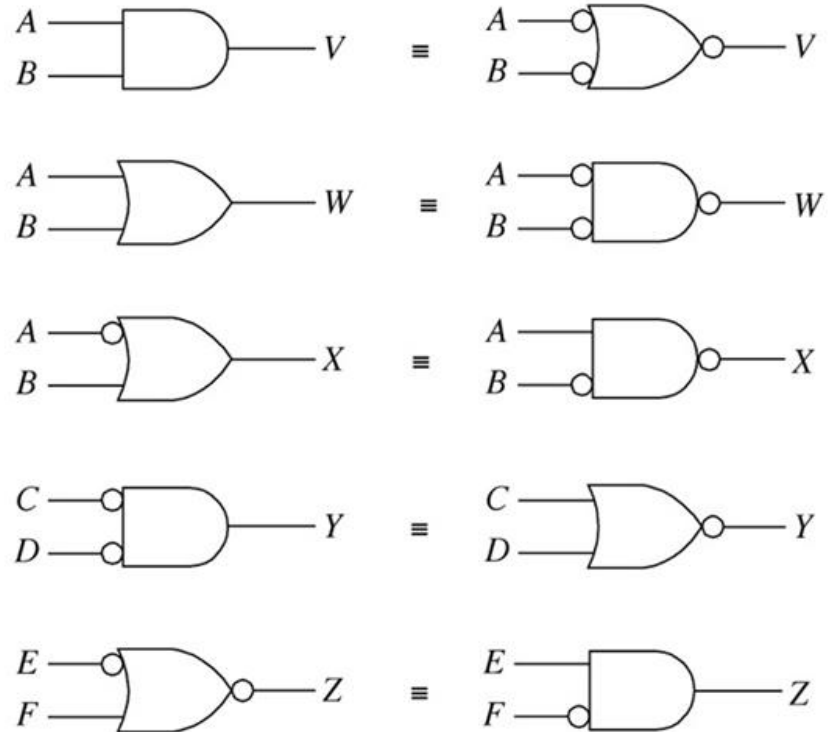1. Place bubble on output of circuit
2. Push bubbles from right to left (output to input) until all bubbles have been pushed to the inputs.
3. When pushing bubbles through a gate, add bubbles where there were none, and remove where there are. Then change gate from AND to OR and OR to AND.



Bubble Pushing Example


Complement F using bubble pushing

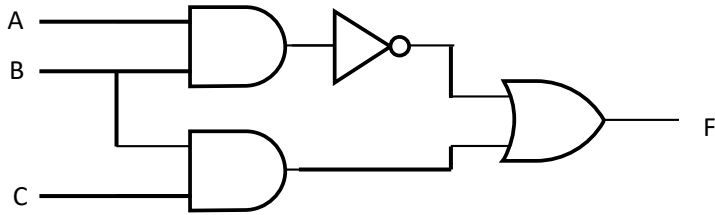

Algebraic check:

$$\begin{aligned}
 F &= \overline{AB} + BC \\
 \bar{F} &= \overline{\overline{AB} + BC} \\
 &= (\overline{\overline{AB}})(\overline{BC}) \\
 &= (AB)(\bar{B} + \bar{C})
 \end{aligned}$$

Answer

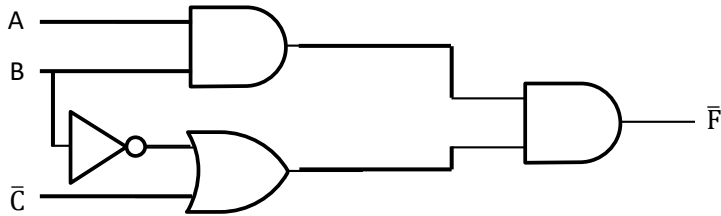

Duals and Self Dual

- A **dual** is an expression in which the
 - OR and AND are exchanged and the
 - 1s and 0s are exchanges
- A **self dual** is when $F = F^D$ where F^D is the dual of F .

Self Dual example

- Example: Is $ab + bc + ac$ self dual?

$$\begin{aligned}
 & ab + bc + ac \\
 &= \overline{\overline{ab + bc + ac}} \\
 &= \overline{\overline{ab} \cdot \overline{bc} \cdot \overline{ac}} \\
 &= \overline{(\overline{a} + \overline{b})(\overline{b} + \overline{c})(\overline{a} + \overline{c})} \\
 &= \overline{(\overline{a}\overline{b} + \overline{a}\overline{c} + \overline{b}\overline{b} + \overline{b}\overline{c})(\overline{a} + \overline{c})} \\
 &= \overline{\overline{a}\overline{b}\overline{a} + \overline{a}\overline{c}\overline{a} + \overline{b}\overline{b}\overline{a} + \overline{b}\overline{c}\overline{a} + \overline{a}\overline{b}\overline{c} + \overline{a}\overline{c}\overline{c} + \overline{b}\overline{b}\overline{c} + \overline{b}\overline{c}\overline{c}} \\
 &= \overline{\overline{a}\overline{b} + \overline{a}\overline{c} + \overline{a}\overline{b}\overline{c} + \overline{b}\overline{c}} \\
 &= \overline{\overline{a}\overline{b} + \overline{a}\overline{c} + \overline{b}\overline{c}} \\
 &= \overline{\overline{a}\overline{b} \cdot \overline{a}\overline{c} \cdot \overline{b}\overline{c}} \\
 &= (a + b)(a + c)(b + c) \text{ Yes, it is a dual}
 \end{aligned}$$

(Involution)

(DeMorgan's)

(DeMorgan's)

(Distributive)

(Distributive)

(Idempotence)

(Consensus theorem)

(DeMorgan's)

Summary

- Logic operators: AND, OR, NOT, NAND, NOR, XOR
- Plug in values to circuit or Boolean expression find truth table
- Boolean identities allow you to simplify Boolean algebras

References

- <https://www.cs.ucr.edu/~ehwang/courses/cs120a/00winter/minterms.pdf>

Copywrite note

- Some of the content of these slides was derived from © 2004 by Pearson Education, Inc. from here:

https://redirect.cs.umbc.edu/courses/undergraduate/CMSC313/fall06/burt/slides/LCDF3_Chap_02_P1.ppt

- Enough of the slides have been altered for the content on these slides to be considered fair use and not “derivative work”.