

Adders and other circuits

CMSC 313
Raphael Elspas

1-bit Adder logic

- Let's build a circuit which adds 2 bits: "a" & "b" together.
- We need two bits to store the output, so we'll use a sum bit "s" and a carry bit "c".

a	b	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$c = ab$$

$$s = a\bar{b} + \bar{a}b = a \oplus b$$


1-bit Adder circuits

- Input: a, b. Output: c, s

a	b	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0



$$c = ab$$

$$s = a\bar{b} + \bar{a}b = a \oplus b$$

 

Abstract it

  - Let's put it in a box called a **block diagram** and call it a half-adder
- **Half-Adder** (HA) definition: adds two 1-bit values and produces a sum bit and a carry bit.
- A full adder should be able to have a carry in, not just a carry out



Full adder motivation

- We want to attach multiple 1-bit adders together to create many-bit adders
- To do this we need a carry-in bit that the previous block's carry-out bit would feed into.

Full Adder

- A Full Adder (FA) has 3 inputs: two 1-bit values and a carry in, and 2 outputs: a sum bit and a carry bit.
- That means we need to add three 1-bit values

A	B	C_{in}	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full Adder

- Algebraically simplify
- Lets try to get similar statements to the Half adder to see if we can repurpose a half adder box.

A	B	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\begin{aligned}
 S &= \bar{A} \bar{B} C_{in} + \bar{A} B \bar{C}_{in} + A \bar{B} \bar{C}_{in} + A B C_{in} \\
 &= \bar{A} (\bar{B} C_{in} + B \bar{C}_{in}) + A (\bar{B} \bar{C}_{in} + B C_{in}) \\
 &= \bar{A} (B \oplus C_{in}) + A (\overline{B \oplus C_{in}})
 \end{aligned}$$

$$S = A \oplus B \oplus C_{in}$$

$$\begin{aligned}
 C_{out} &= \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC \\
 &= C(\bar{A}B + A\bar{B}) + AB(\bar{C} + C)
 \end{aligned}$$


$$C_{out} = C(A \oplus B) + AB$$

Full adder realized circuit

- Convert to a circuit

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = C_{in} (A \oplus B) + AB$$

 


Full adder realized circuit

- Convert to a circuit


$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = C_{in} (A \oplus B) + AB$$

 


thanos

Full adder

 


Half adder

 


Full Adder

 - 3 Inputs: A, B, Carry in
- 2 outputs: Sum, Carry out
- Put it in a box!




Ripple Carry Adder

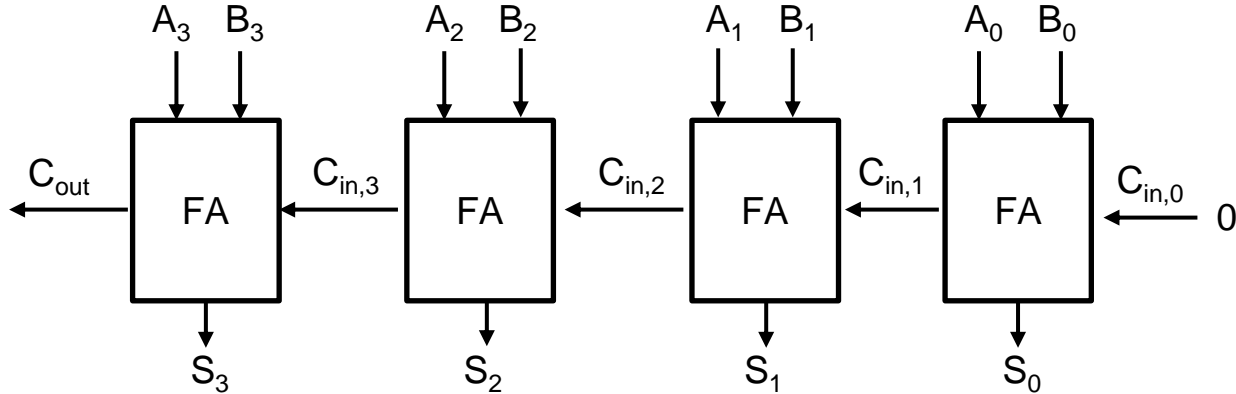- Chain together Full Adders to add multiple bits
- $C_{in,0}$ is set to 0, since nothing is being carried in



Ripple Carry Adder example

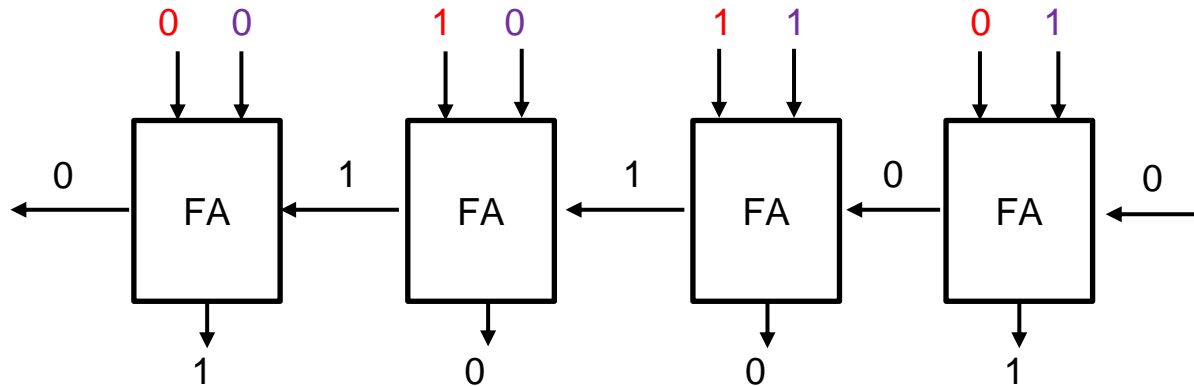- $A_3A_2A_1A_0 = 0110$ (6)
- $B_3B_2B_1B_0 = 0011$ (3)



Result: 1001, Carry 0

Check: $6+3 = 9$


Ripple Carry Adder - 2s complement

- Does this module work for 2s complement?
- Yes! Because 2s complement uses regular addition
- But the number has to already be in 2s complement form
- Lets try $-5 + 3$

Ripple Carry Adder - 2s complement example

 (5) $0101 \rightarrow (\text{inv}) \rightarrow 1010 \rightarrow (+1) \rightarrow 1011$

- $A_3A_2A_1A_0 = 1011$ (-5)
- $B_3B_2B_1B_0 = 0011$ (3)




Result: 1110, Carry 0

Check: 1110 (2s complement)
 1101 (-1)
 0010 (invert bits)
 = -2


It works!

- Let's put it in a box

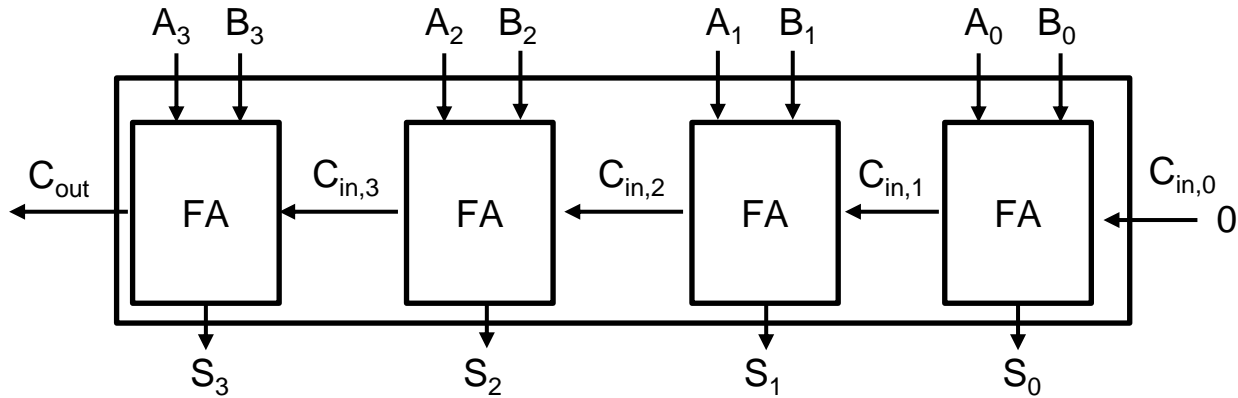


- $C_{in,1}$ - $C_{in,3}$ are internal variables, so they disappear


4-bit adder

 

4-bit adder another representation

 


Note

 

Means there are four wires here—called a “bus”


8-bit adder from 4 bit adder

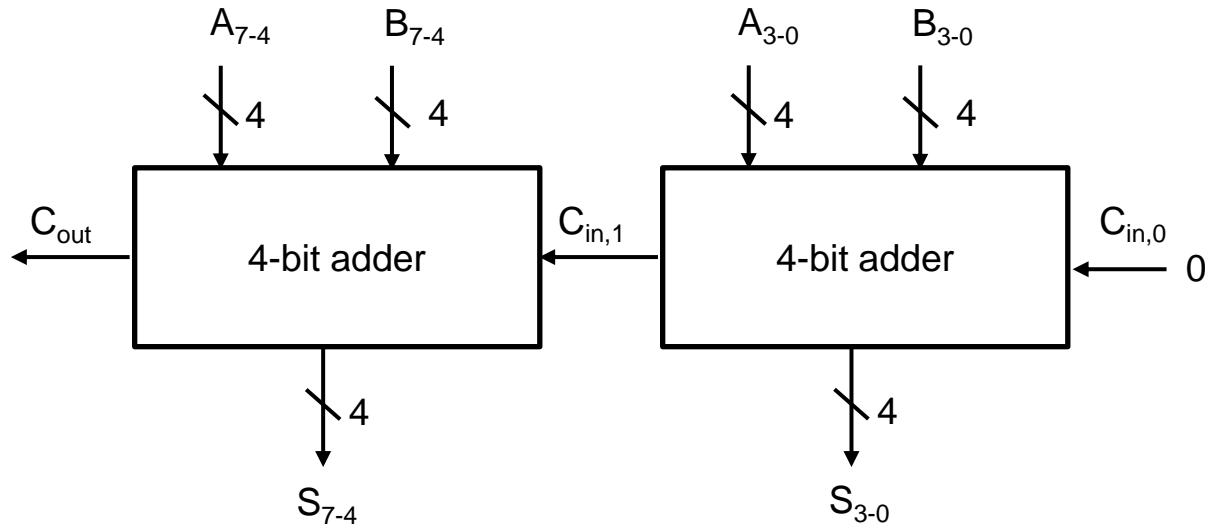



Adder-Subtractor

- In order to make a subtractor, we have to make a 2's complement converter.
- Then we'll reuse the adding circuit as before
- In order to do $A - B$, we'll convert the B to 2's complement – but we also want to be able to add $A + B$. We need a switch to turn subtracting on and off.
- In subtractor mode, we need to invert the bits in B and add 1
 - We can make a controllable inverter with an XOR gate
 - We can add 1 with the Carry-in to the first FA.

Adder-Subtractor implementation

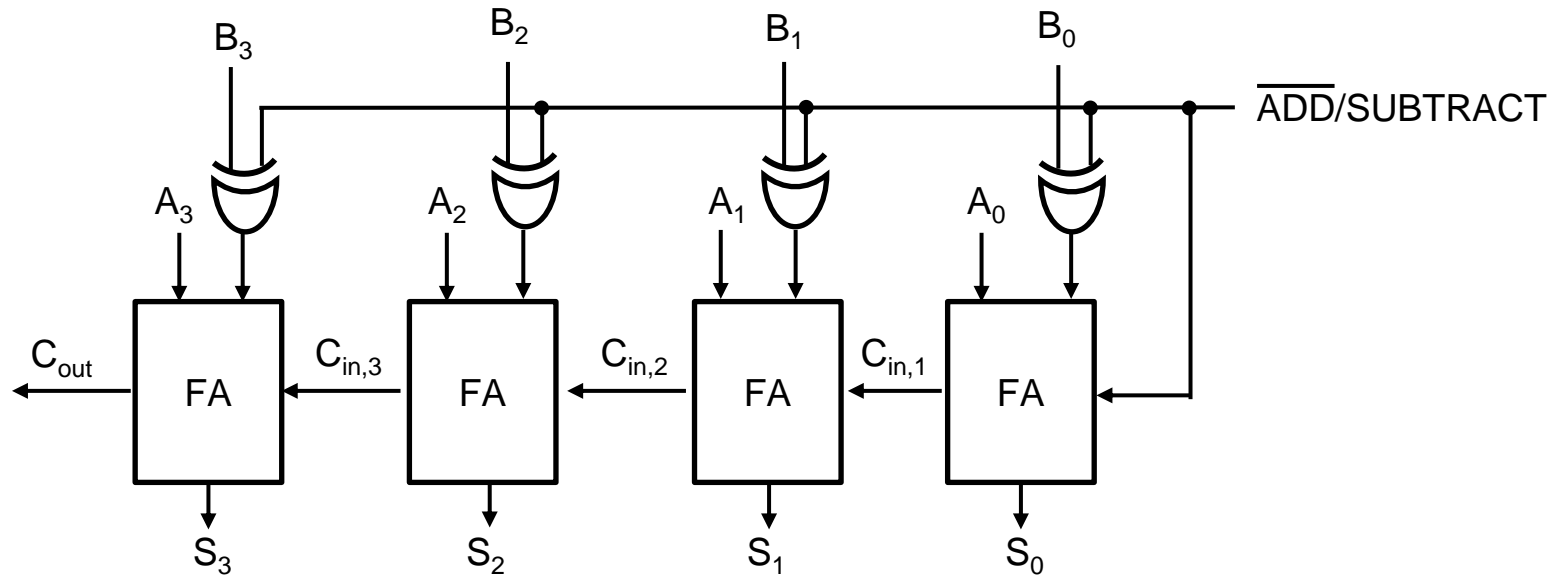


Ripple Carry adder delay

 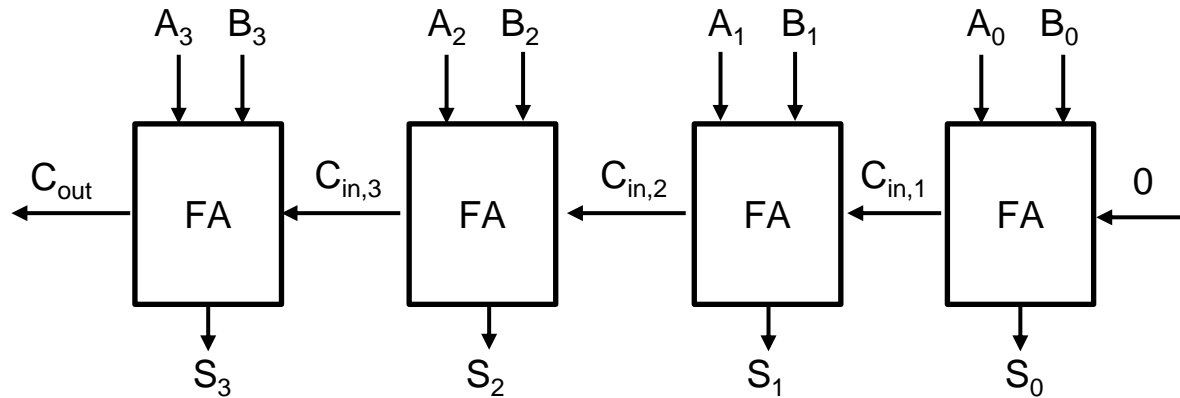


Gate Delay

 - Every gate incurs some delay as information passes through.
- We want to minimize circuit delay so that circuits are faster
- We measure worst delay from the **critical path**. This is the longest path from input to output in terms of number of gates traversed.




The two critical paths pass through 3 OR gates

Ripple Carry adder delay

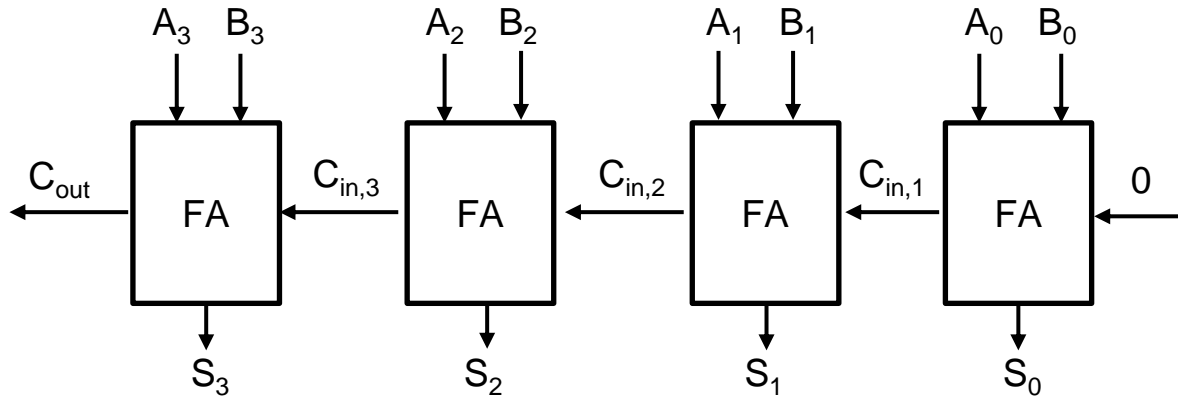

Full Adder

 

Critical Paths for Full Adder:


$A, B \rightarrow C_{out}$: 3 gates

$C_{in} \rightarrow C_{out}$: 2 gates

$A, B \rightarrow Sum$: 2 gates


$C_{in} \rightarrow Sum$: 1 gate

Ripple Carry adder delay

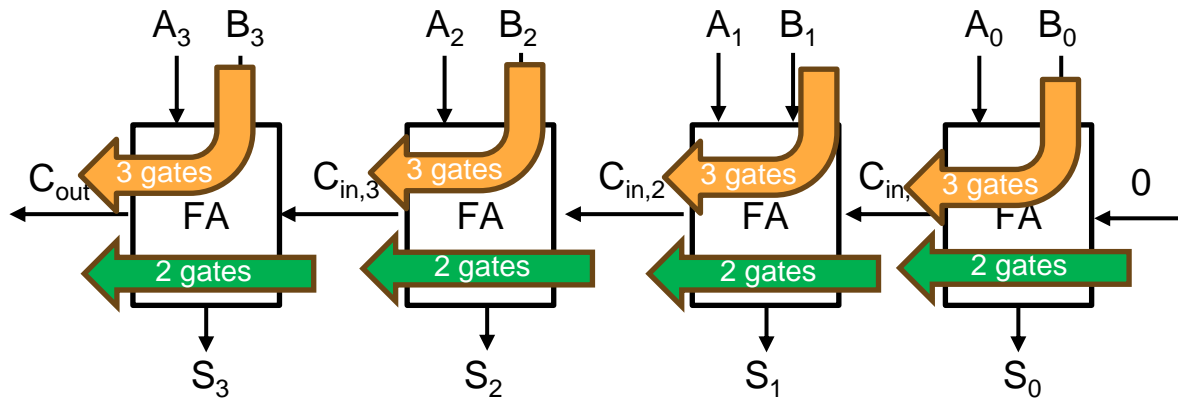

All paths displayed

Full Adder

 

Paths for Full Adder:



A, B → C_{out} : 3 gates

C_{in} → C_{out}: 2 gates

A, B → Sum: 2 gates

C_{in} → Sum: 1 gate

Ripple Carry adder delay

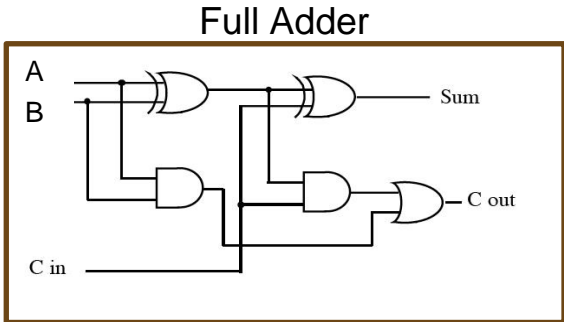 

Paths for Full Adder:

A, B \rightarrow C out : 3 gates

C in \rightarrow C out: 2 gates


A, B \rightarrow Sum: 2 gates

C in \rightarrow Sum: 1 gate

Idea: predict carry in advance

- Predict carry-in value in advance so numbers can be added in parallel
- $C_{in,i}$ for Full adder i relies on all input bits before it including A_0 through A_{i-1} , B_0 through B_{i-1} , and $C_{in,0}$ through $C_{in,i-1}$.
- All Carry in values are dependent on either A or B, so we can leave them out as part of the predictor logic.

Carry lookahead adder idea

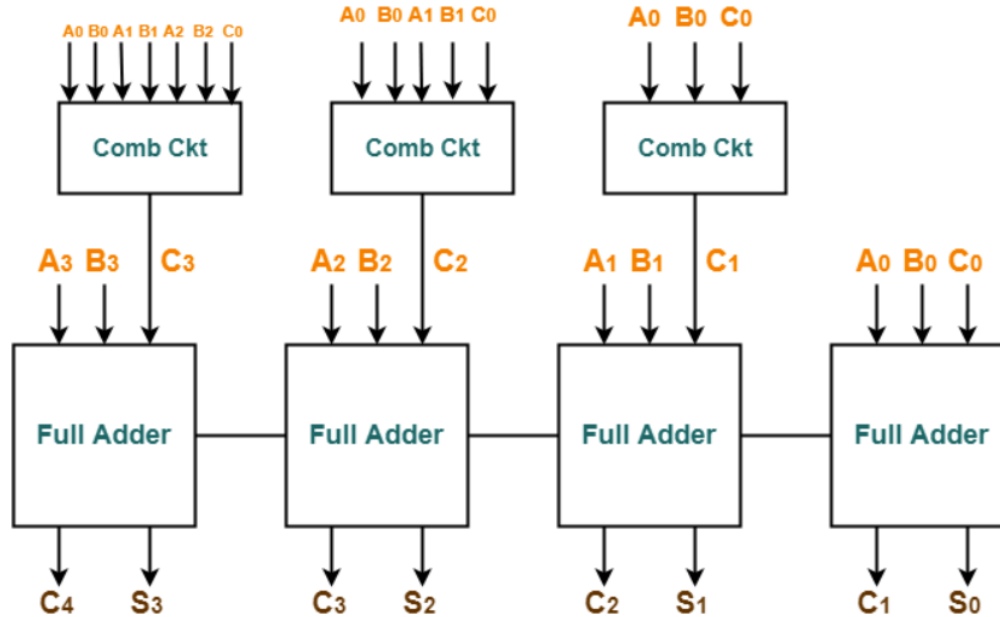


Calculating each carry

- Remember how we calculate carry out in the Full Adder

$$C_{out} = C_{in} (A \oplus B) + AB$$

- We can find each of the carry bits this way, and create expressions that are dependent on previous values

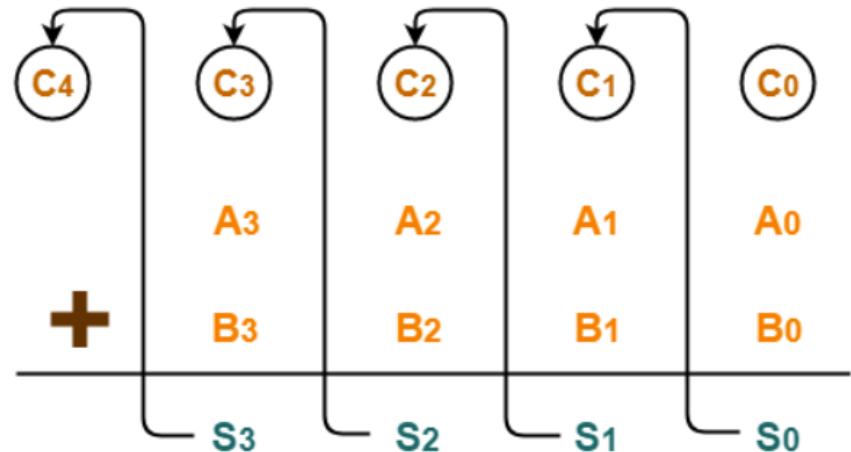- $C_1 = C_0 (A_0 \oplus B_0) + A_0 B_0$
- $C_2 = C_1 (A_1 \oplus B_1) + A_1 B_1$
- $C_3 = C_2 (A_2 \oplus B_2) + A_2 B_2$
- $C_4 = C_3 (A_3 \oplus B_3) + A_3 B_3$



Carry algebra

For simplicity, Let-

- $G_i = A_i B_i$ where G is called carry generator
- $P_i = A_i \oplus B_i$ where P is called carry propagator

Therefore, we'll rewrite each $C_{i+1} = C_i (A_i \oplus B_i) + A_i B_i$ as

- $C_1 = C_0 P_0 + G_0$
- $C_2 = C_1 P_1 + G_1$
- $C_3 = C_2 P_2 + G_2$
- $C_4 = C_3 P_3 + G_3$


Carry algebra

- C_1 , C_2 and C_3 are intermediate carry bits.
- So, let's remove C_1 , C_2 and C_3 from RHS of every equation.
- Substituting $C_1 = C_0P_0 + G_0$ in for $C_2 = C_1P_1 + G_1$ we get C_2 in terms of C_0 .
- We can continue substituting so we get C_3 in terms of C_0 and so on.


Therefore we'll get

- $C_1 = C_0P_0 + G_0$ ← 3 gates delay
- $C_2 = C_0P_0P_1 + G_0P_1 + G_1$ ← 3 gates delay
- $C_3 = C_0P_0P_1P_2 + G_0P_1P_2 + G_1P_2 + G_2$ ← 3 gates delay
- $C_4 = C_0P_0P_1P_2P_3 + G_0P_1P_2P_3 + G_1P_2P_3 + G_2P_3 + G_3$ ← 3 gates delay


Carry Lookahead adder

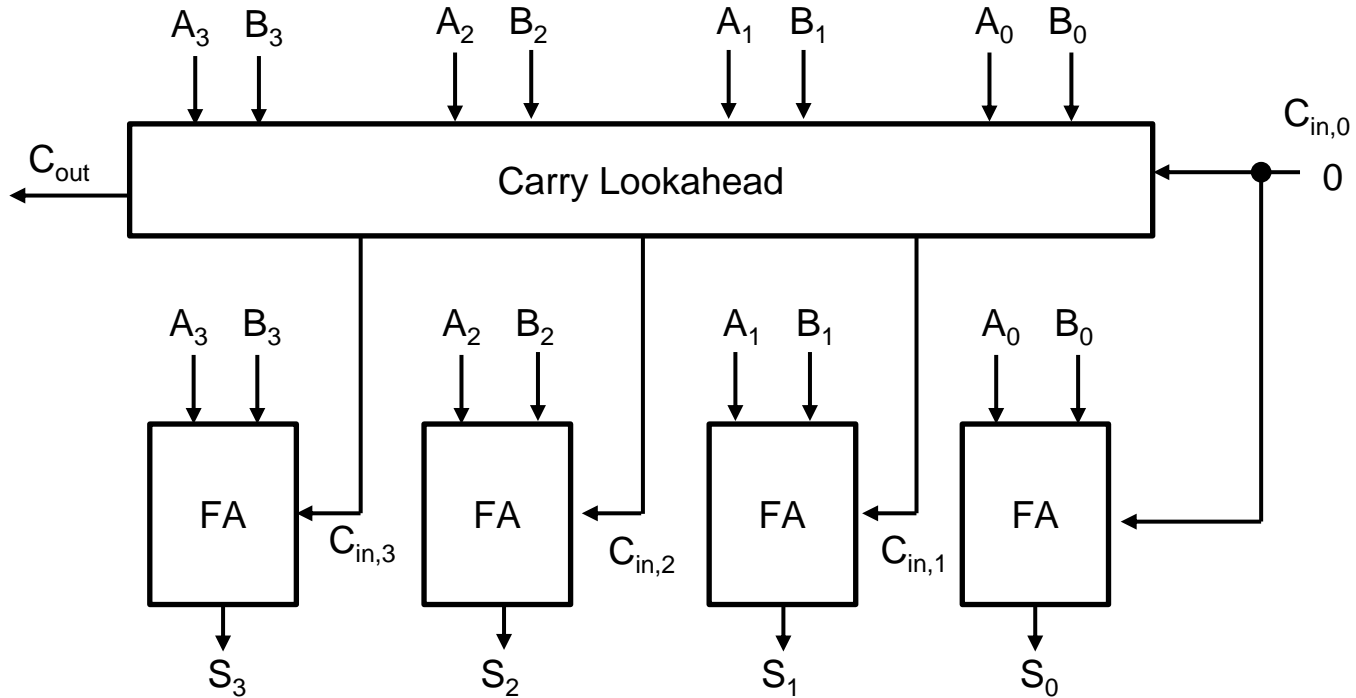


Carry Lookahead adder

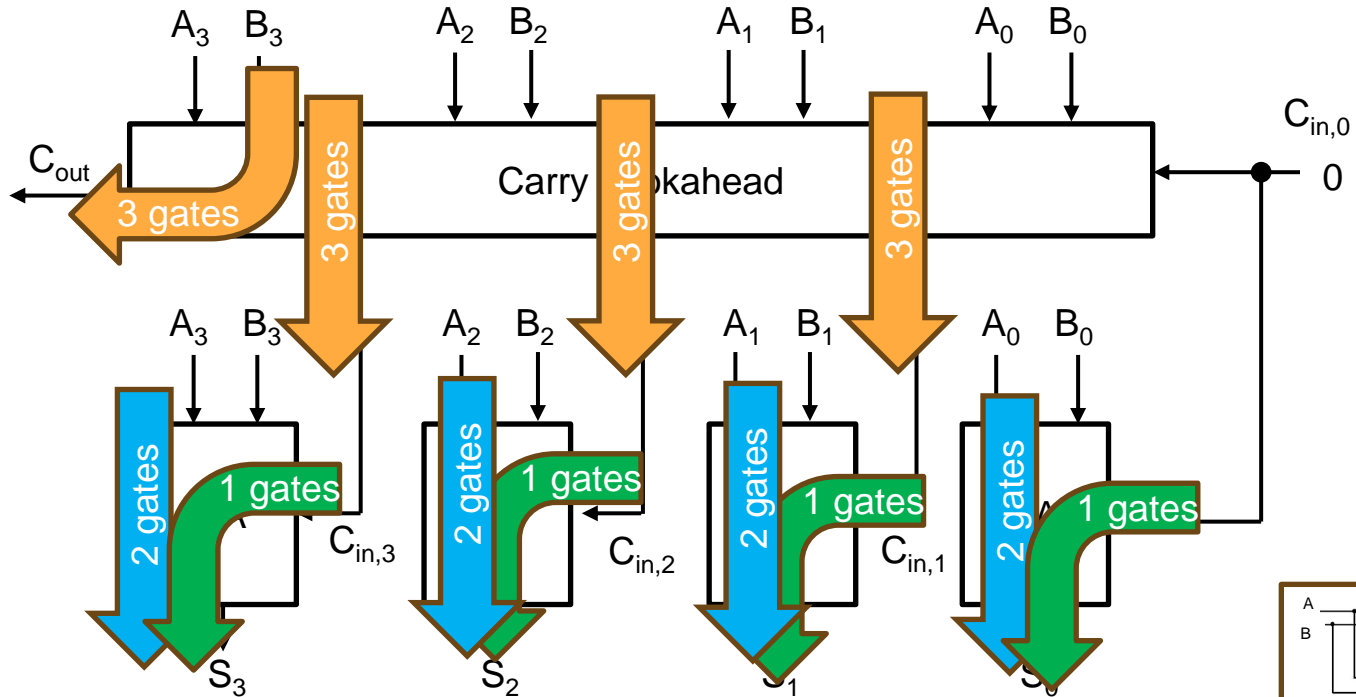

Full Adder

 


Carry Lookahead adder

 

Critical Path:
4 gates


Decoder (DEC)

 - A Decoder is a circuit that has n inputs and 2^n outputs.
- A decoder converts a binary number $s = s_{n-1}s_{n-2}\dots s_1s_0$, and produces a “1” on the decoded line F_s , and “0” on all other F output lines.
- Decoders are a combinational circuit that appear frequently in computer hardware and ALUs




Decoder example

 
If s_1s_0 equals 10, (or 2 in decimal), then F_2 will equal 1 and the other F s equal 0.



2-bit Decoder (DEC)

 


s_0	s_1	F_0	F_1	F_2	F_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 


Multiplexer (MUX)

 - A multiplexer (MUX) has n select bits “ s ” which allow you to select one of the 2^n input lines “ I ” to duplicate on the output line “ out ”
- Basically allows different inputs to share the same wire as an output
- Use a trapezoid to represent MUX



4-input MUX example

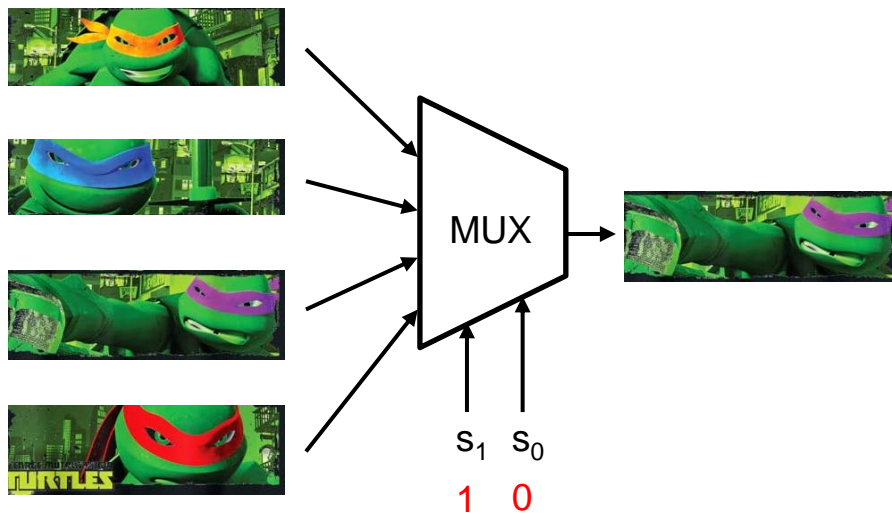
- If I select $s=10$, then I'm selecting the second line to be displayed on the output




4-input MUX example explanation

- 6 inputs, so truth table would have 64 rows
- We need an efficient way to design this

s_1	s_0	out
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 


Elon MUX

 


2-input gate level implementation MUX

s	I ₀	I ₁	out
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 


		I ₀ I ₁			
		00	01	11	10
s	0	0	0	1	1
	1	0	1	1	0

$$F = \bar{s}I_0 + sI_1$$

 


Chain MUXes

 Easier than making 6 input Kmap (4 input, 2 select).




Demultiplexer (DEMUX)

 - A demultiplexer (DEMUX) does the inverse of a MUX.
- A DEMUX has n select bits “ s ” which allow you to select one of the 2^n output lines to copy the input line to
- Basically allows an input to split an output on different wires.



DEMUX example

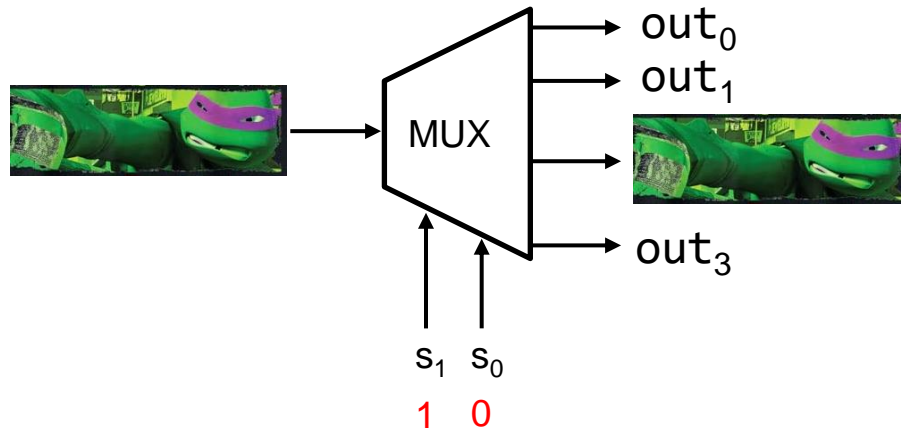- If I select $s=10$, then I'm selecting the second line I_2 to be displayed on the output
- All other outputs have nothing sent over them



DEMUX implementation

- Two different representation of the truth table


in	s_1	s_0	o_0	o_1	o_2	o_3
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

s_1	s_0	o_0	o_1	o_2	o_3
0	0	in	0	0	0
0	1	0	in	0	0
1	0	0	0	in	0
1	1	0	0	0	in

ALU

- **Arithmetic logic unit (ALU)** is a combinational digital circuit that performs arithmetic and bitwise operations on integer binary numbers.

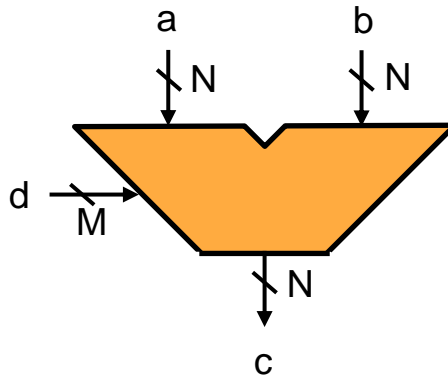a,b are integer operands
 c is an integer result
 d is an operation selector



N: the width of the inputs and outputs of the ALU.
M: the width of the operation selector. There are 2^M operations for a selector that has a width of M.

Summary

- Half adder IN(a,b) OUT(c_{out} , sum)
- Full adder IN(a,b, c_{in}) OUT(c_{out} , sum)
- Carry lookahead adder reduces cumulative gate delay
- Decoder outputs a 1 on a specific wire, and 0 everywhere else
- Multiplexer and Demultiplexer convert multiple wires to share one line and the reverse respectively.

References

- <https://www.gatevidyalay.com/tag/disadvantages-of-carry-look-ahead-adder/>
- <https://www.allaboutelectronics.org/half-adder-and-full-adder-explained/>
- <https://redirect.cs.umbc.edu/~tsimo1/CMSC313/topics/Slides21.pdf>