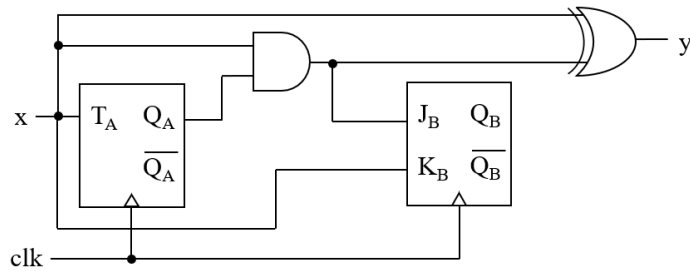



CMSC 313 Spring 2024

Practice questions for Quiz 3

Exercise 1. Given the circuit below:



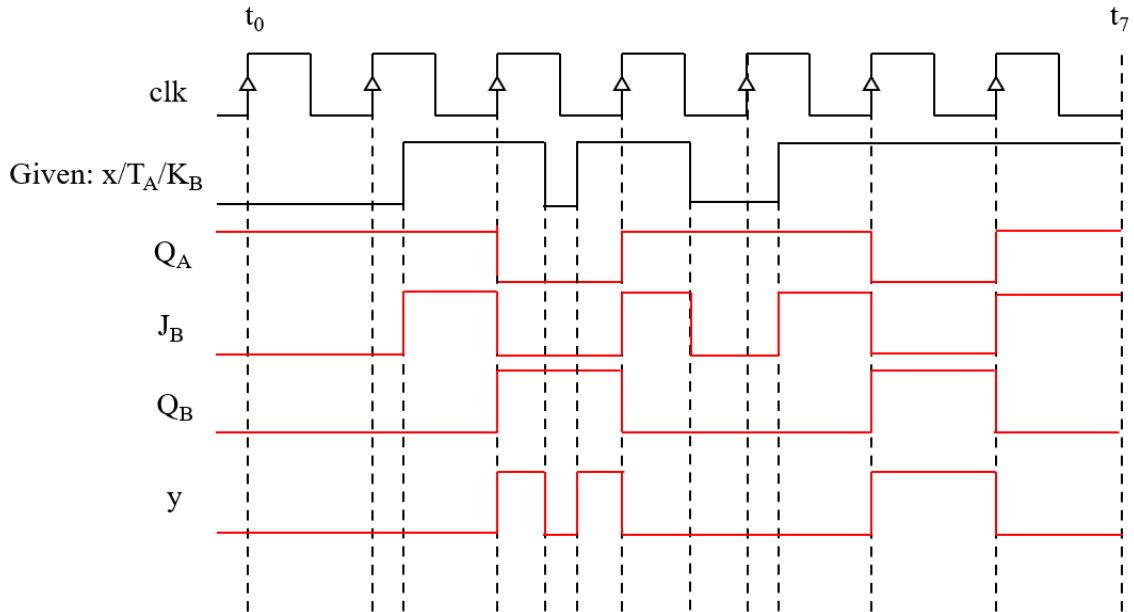a. Given input x in the trace, find Q_A , J_B , and Q_B .



b. Find the state equations $Q_A(t+1)$ and $Q_B(t+1)$ and output y in terms of x , $Q_A(t)$, $Q_B(t)$.

Step 1

$$\begin{aligned} T_A &= x \\ J_B &= xQ_A(t) \\ K_B &= x \end{aligned}$$


Step 2

$$\begin{aligned} Q_A(t+1) &= T\overline{Q_A(t)} + \overline{T}Q_A(t) \\ Q_B(t+1) &= J\overline{Q_B(t)} + \overline{K}Q_B(t) \end{aligned}$$

Step 3

$$\begin{aligned} Q_A(t+1) &= x\overline{Q_A(t)} + \overline{x}Q_A(t) \\ Q_B(t+1) &= xQ_A(t)\overline{Q_B(t)} + \overline{x}Q_B(t) \\ y &= x \oplus (xQ_A(t)) \end{aligned}$$

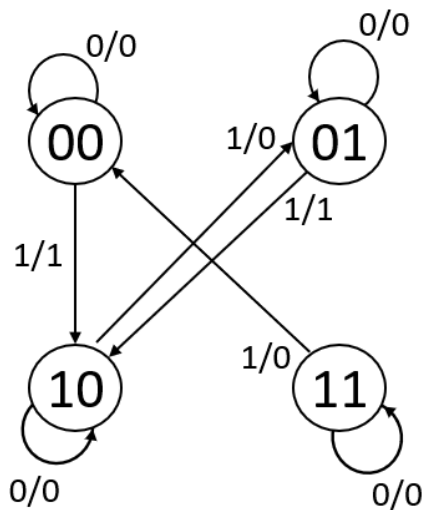b. Complete the state table and complete the state diagram.



| x | Q_A | Q_B | Q_{A+} | Q_{B+} | y |
|---|-------|-------|----------|----------|---|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 |