

CMSC 313 Spring 2024



Quiz 3 Answers

Full Name _____ Student ID _____


For every exercise, show your work. Not showing complete work may result in penalties.

Exercise 1. (10 pts) Draw the traces for the following circuit. Before t_0 ,

$$x = 1, Q_A = 0, J_B = 1, Q_B = 0$$

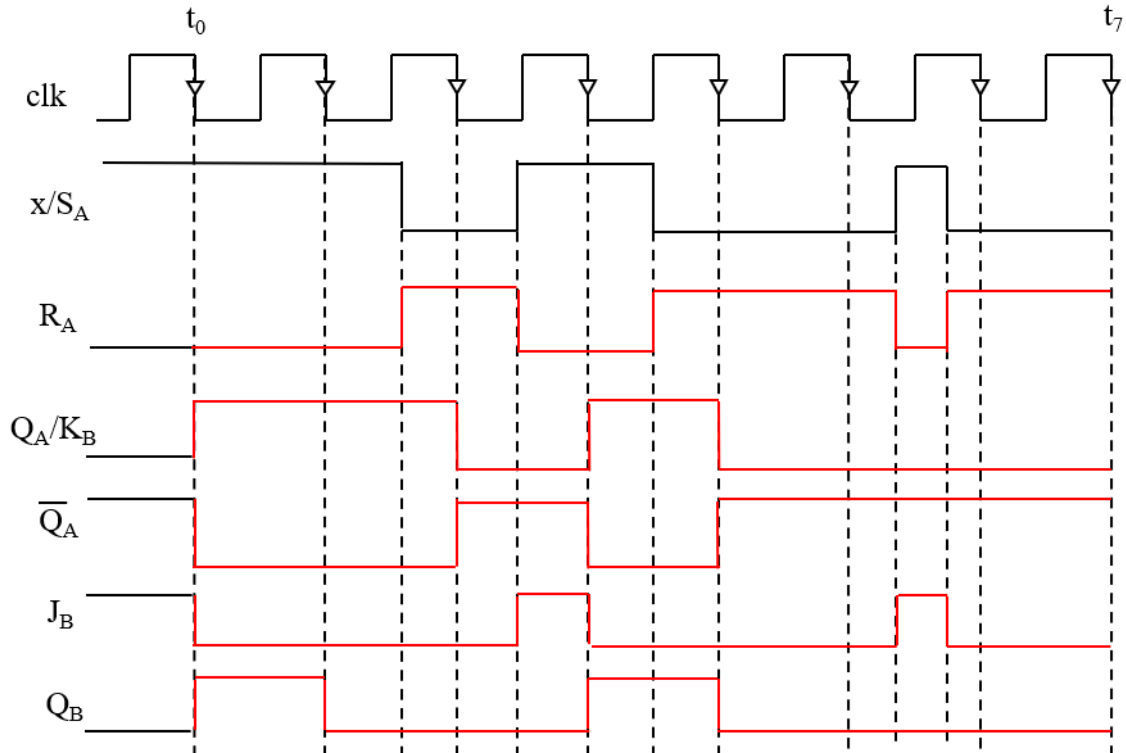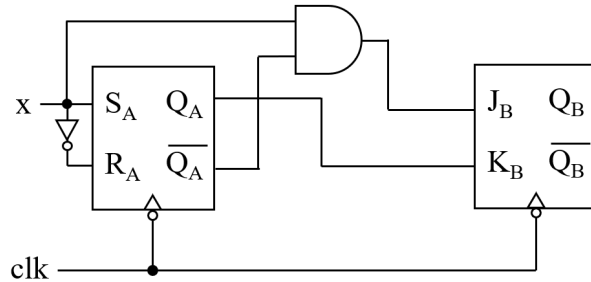

Exercise 2. Given the circuit:

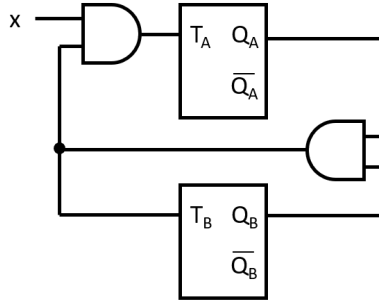

a. (10 pts) Find the state equations $Q_A(t+1)$ and $Q_B(t+1)$ in terms of x , $Q_A(t)$, $Q_B(t)$. Box your final answer.

Step 1

$$T_A = xQ_A(t)Q_B(t)$$

$$T_B = Q_A(t)Q_B(t)$$

Step 2

$$Q_A(t+1) = T\overline{Q_A(t)} + \overline{T}Q_A(t) = T \oplus Q_A(t)$$

$$Q_B(t+1) = T\overline{Q_B(t)} + \overline{T}Q_B(t) = T \oplus Q_B(t)$$

Step 3 (I said they did not have to simplify)

For solutions with \oplus they need to group operands with parenthesis.

$$Q_A(t+1)$$

$$= xQ_A(t)Q_B(t)\overline{Q_A(t)} + \overline{xQ_A(t)Q_B(t)}Q_A(t)$$

$$= xQ_A(t)Q_B(t)Q_A(t)$$

$$= (xQ_A(t)Q_B(t)) \oplus Q_A(t)$$

} Any of these solutions are valid

$$Q_B(t+1)$$

$$= Q_A(t)Q_B(t)\overline{Q_B(t)} + \overline{Q_A(t)Q_B(t)}Q_B(t)$$

$$= Q_A(t)Q_B(t)Q_B(t)$$

$$= (Q_A(t)Q_B(t)) \oplus Q_B(t)$$

} Any of these solutions are valid

Must use parenthesis with \oplus

Must use parenthesis with \oplus

b. Complete the state table (10 pts) and complete the state diagram (10 pts).

x	Q_A	Q_B	Q_{A+}	Q_{B+}
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	0	1
1	1	0	1	0
1	1	1	0	0

